
 


# PCB Amplifier Preliminary Results

 


# Noise

- Noise present in all amplifier channels
  - 200+ MHz frequency
  - ~200-400 mV peak-peak
  - Easily filtered by oscilloscope low-pass filter
- Noise is notably present in ground and power planes of the PCB
  - Phase relationship between oscillation, probed at various locations, suggests full-board synchronized oscillation...





# Source of Noise

 - -2.5V, GND, and +2.5V provided by terminals at board edge
  - Distributed to components through planes
- Parasitic resistances and inductances
  - Naturally present in board



  
# Source of Noise, cont'd


- When transient current is drawn by the op-amp, due to any fluctuation, current must travel to edge of board
  - Natural capacitance between planes is insufficient to source enough current
- Impedance along large loop creates voltage shifts in the ground plane and  $V+/V-$  planes
  - Power supply rejection ratio (right) decreases at high frequency
  - All signals are referenced w.r.t ground, thus...
- Feedback loop causing stable oscillation
  - Spans board in-phase (w/ speed-of-light delay)


 
# Adding a Decoupling Capacitor

- High capacitance, low series resistance and impedance, capacitor between GND and V+/V- vias
  - Stabilizes planes against transient fluctuations
  - Planes only conduct DC/low frequency current
- Current loop avoids resistive & inductive impedance of planes, preventing feedback and cross-talk of noise




 


# Characterization of Channel Responses

# Determining Parasitic Input Capacitance


Expected Fall Time Constant (Input Capacitor)	Measured Fall Time Constant (Eff. Total Cap.)
50 ns (2 pF)	130(10) ns (2 + 3.2(4) pF)
100 ns (4 pF)	170(10) ns (4 + 2.8(4) pF)
200 ns (8 pF)	270(20) ns (8 + 2.8(8) pF)
200 ns (16 pF)	240(10) ns (16 + 3.2(8) pF)

 


Channel 20

 

Channel 3

 

Channel 16

 

Channel 17


# Determining Parasitic Input Capacitance, cont'd

- Thus, parasitic input capacitance  $\approx 3.0(3)$  pF
- LTC 6269-10 op-amp input capacitance specified as  $\sim 0.45$  pF
- Thus,  $\sim 2.5$  pF of input capacitance unaccounted for
  - Potential sources include PCB traces, solder pads, input wires to terminals, vias
- Effects of parasitic input capacitance:
  - **Change in the amplifier current-to-pulse-height gain (proportional to  $C_{\text{parasitic}}/C_{\text{in}}$ )**
  - Change in falling time constant (proportional to  $C_{\text{parasitic}}/C_{\text{in}}$ )
- Thus, may cause some constant offset & some variance between channels, in the amplifier gain
  - Can be minimized by increasing  $C_{\text{in}}$ , but this imposes other restrictions on gain and shaping


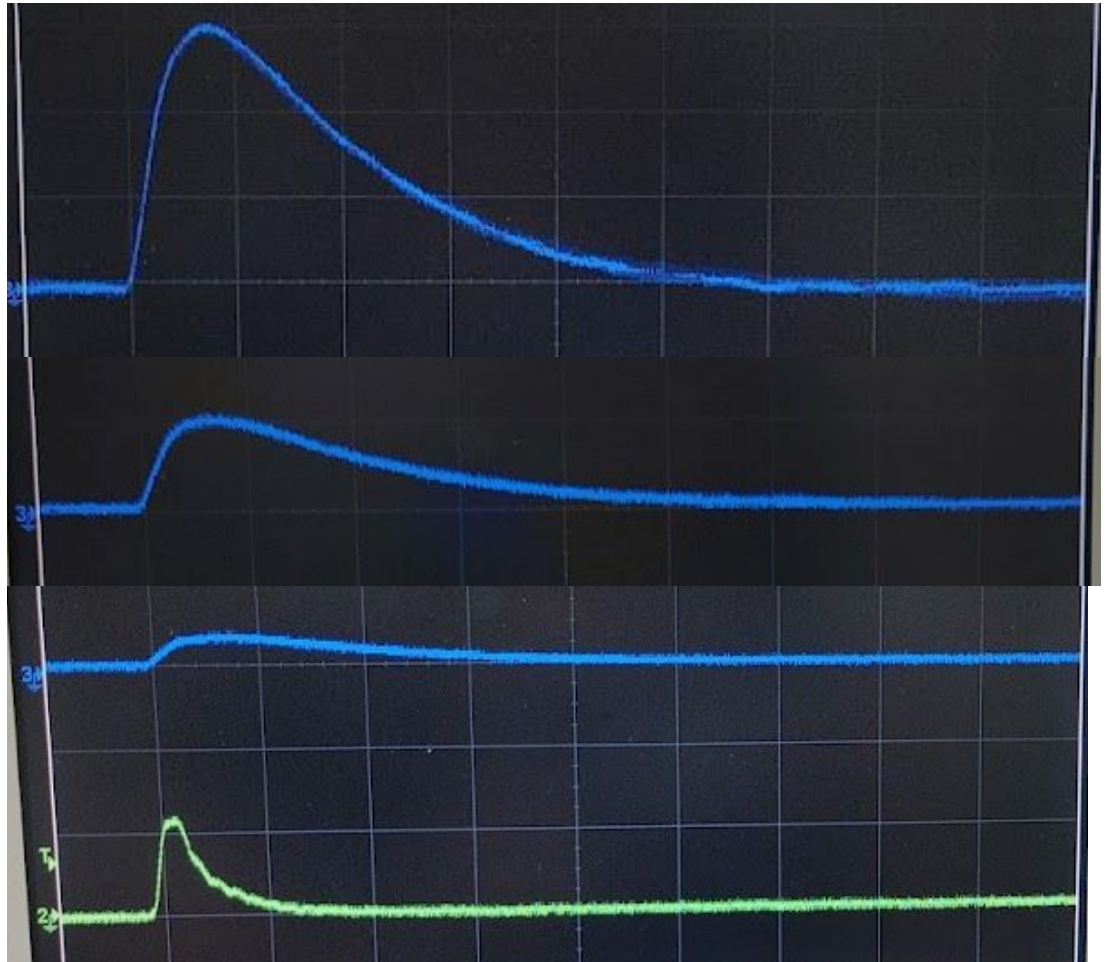
# Gain Settings

- Channels 3-5
  - 4 pF  $C_{in}$  (+ 3 pF par.)
  - Gains 10x, 33x, 100x
- Gain-Bandwidth product limitation of  $\sim 4$  GHz
  - In theory, introduces signal delays dependent on gain
  - On order of 0.4 ns, 1.3 ns, 4 ns
  - Initial characterization (right) was 100 ns/div, need further characterization to determine if delays are present
  - Would introduce timing variations dependent on chip-to-chip variation of GBWP



# Conclusion

- With reasonably high confidence, oscillatory noise from PCB plane current loops should be dramatically reduced or eliminated by adding decoupling capacitors to the PCB design, located at each op-amp
  - Sustained oscillation requires loop gain  $> 1$ , at 400 MHz op-amp gain alone is only 10x
  - Decreasing impedance between  $V+/V-$  and ground by even 10x will likely prevent oscillation
- Parasitic capacitance ( $\sim 3$  pF) present on all inputs
  - Can be accounted for in final design
  - Recommend total (discrete + parasitic) input capacitance 6-8 pF, to achieve reasonable gain and resistance to variation due to channel-to-channel differences in parasitic capacitance
- Gain appears to have minimal issues with delays/bandwidth issues
  - Need some further investigation
  - Even with maximum 4 ns delay, a 10% chip-to-chip variance would only create  $\sim 0.4$  ns variance in event delay